


CS/EE 181a 2010/11 Lecture 5

General topic of today's lecture: *Time*.

- Clocks
- Registers
- Maintaining value over time (Charge sharing, leaking)

Where We Are

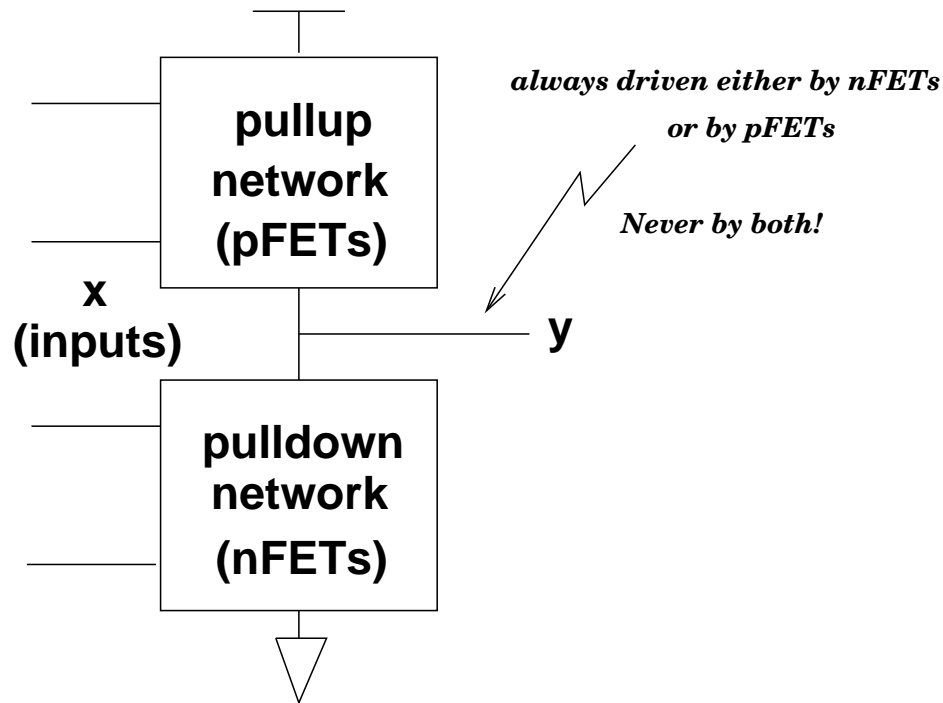So far, we have spoken only of logic with no mention of *time*:




Analyze nFET network

Analyze pFET network

- Canonical sum-of-products
- K-maps
- Quine-McCluskey
- Gate sharing ...

The Golden Rules

(for static CMOS design)

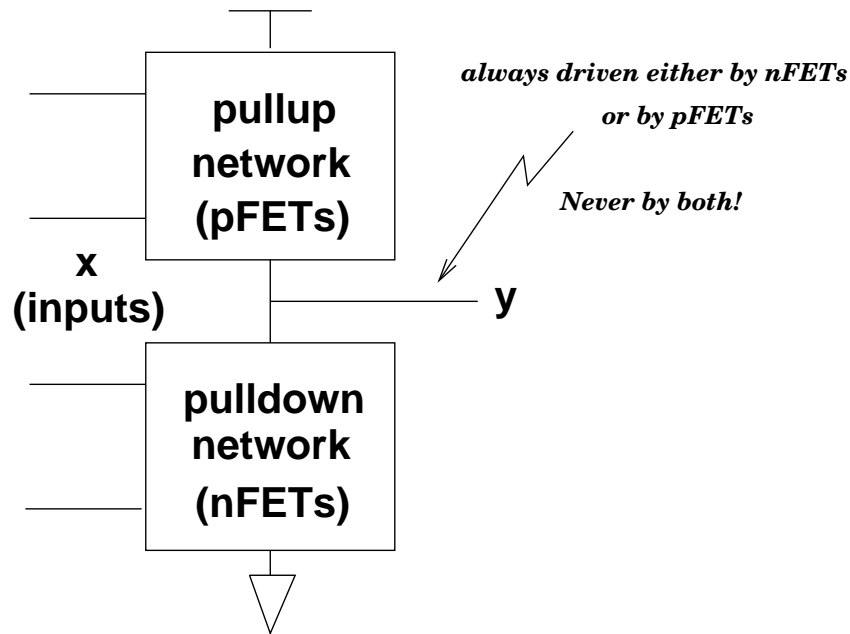

Four rules:

- Highs passed by pFETs.
- Lows passed by nFETs.
- Output always driven.
- No short circuits between the power supplies.

How (and when) do we change the outputs?

How Do We Design Large Systems?

- One big combinational circuit implementing a big function...? Impossible: size!
- Notion of *algorithm*: Sequence of steps, repetition trading size for execution time
- Notion of *pipelining*: Most algorithms (Systems) are used to compute a sequence of outputs for a sequence of inputs (with or without dependencies on each other)

$$\dots x_3, x_2, x_1 \rightarrow [F] \rightarrow F(x_3), F(x_2), F(x_1)\dots$$

Assume $F = k.h.g$. Pipelining is possible:

$$x_4 \rightarrow [g] \rightarrow g(x_3) \rightarrow [h] \rightarrow h.g(x_2) \rightarrow [k] \rightarrow k.h.g(x_1) \blacksquare$$

Throughput improved, latency worse!

Sequencing

- In hardware, concurrency (doing things in parallel) is easier than sequencing...

$$y := f(x); z := g(y); w := h(z)$$

- When do we know that f has finished computing y and g can use it to compute z ? Two solutions:
- Use time: Clocked design (this term)
- don't use time...: asynchronous, clockless (next term)

Using Clocks for Sequencing

$$y := f(x)$$

- We introduce clock signals ϕ and ϕ' such that x is valid at ϕ and y is valid at ϕ' . We know and control δ :

$$t(\phi') - t(\phi) = \delta + \epsilon$$

where ϵ is the *clock skew*.

- We choose δ such that the time it takes to compute $f(x)$ is less than $\max(\delta + \epsilon)$ for all x
- Not only time constraint... More depending on choice of clock signals ϕ and ϕ' .

Two Basic Schemes

- Add the clock signal to the function: $y := f(x) \wedge \phi$
precharge, dynamic, domino-style...


(modern, for later...)

- Add the clock signal to the input:

$$x' := x \wedge \phi \parallel y := f(x') \parallel y' := y \wedge \phi' \parallel z := g(y') \dots$$

Separate latching of inputs. (traditional, safe, for now...)

 How do we keep floating values over time?




What happens? Recall

$$R_{\text{off}}/R_{\text{on}} \approx 10^5 \dots$$

Thus: $\tau_{\text{off}}/\tau_{\text{on}} \approx 10^5$ as well. In other words, a *long* time. We will use this soon...

Timing

 

Obviously, we need *some* notion of time so we can use the circuit repeatedly.

- Unambitious goal: Use combinational logic more than once. (As often as possible.)
- More ambitious goal: Trade circuit size for execution time.

This brings us to the two uses of clocks (or other means of synchronization):

- Circuit timing.
- Sequencing of algorithms.

This is what keeps VLSI interesting.


Ways to approach the problem

To use a circuit repeatedly, we want to make sure that we give it enough time to compute its outputs.

General approach: Issue inputs to circuit, wait for it to be done computing, then look at the result.

How to accomplish the “wait for it to be done computing”?

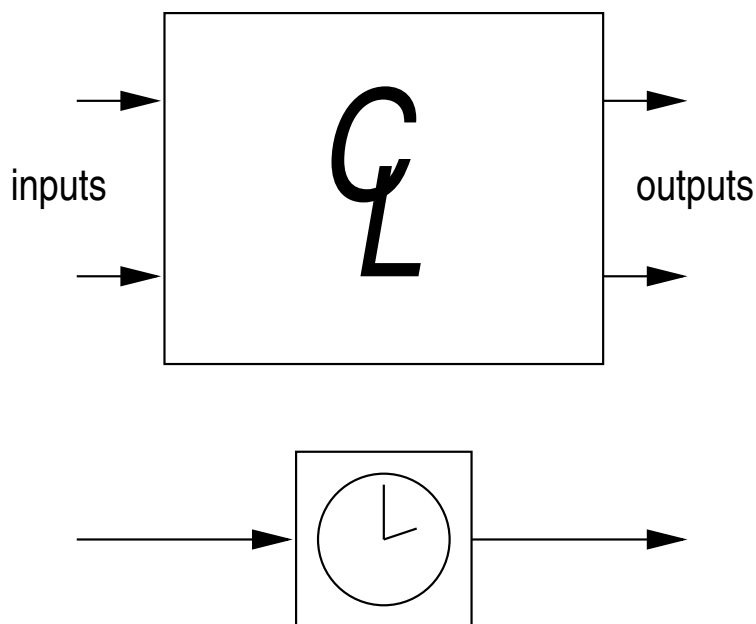
Use a timer? (Asynchronous bundled data protocol.)



This works, but it's not used very much. . .

Let the data do its own timing

 We can make the “appearance” of output data signal that the computation is done.



output \Rightarrow validity

There are some subtle issues here:

- For starters, how do we know that the computation is done if the result is the same as the last time we used the circuit?
- Leads to handshake protocols. This happens for the bundled method too.
- No glitches allowed (at least on the outputs)!


See CS/EE 181 b, CS185 for more about this. . .

Another issue—glitches

Why is it hard to know when a circuit is “done”? Can we just wait for the output to change?

- Yes, but this requires a lot of care. . . (More than we are willing to invest right now.)

Example. Implement:

 


What happens when z changes?

time	x	y	z	$w = z'$	$f = xz + yw$
0	1	1	1	0	1
1	1	1	0	0	0
2	1	1	0	1	1

How to get rid of glitches

The $f = xz + yz'$ has a nasty glitch.

 

How can we get rid of this?


- In this particular case, we can cover an “extra” implicant. Makes circuit safe for any single input changing.
- Can’t fix it for general input changes!

Two ways out:

- Restricting our attention to classes of circuits that do not glitch. (This is a rather severe restriction—next term)
- Allowing the circuit to glitch, but ignoring it during that time. (“Wait until the outputs are ready.”) Hopefully, it will eventually stabilize. . .
- Can be expensive in terms of energy in large combinational blocks. . .

For now—clocks

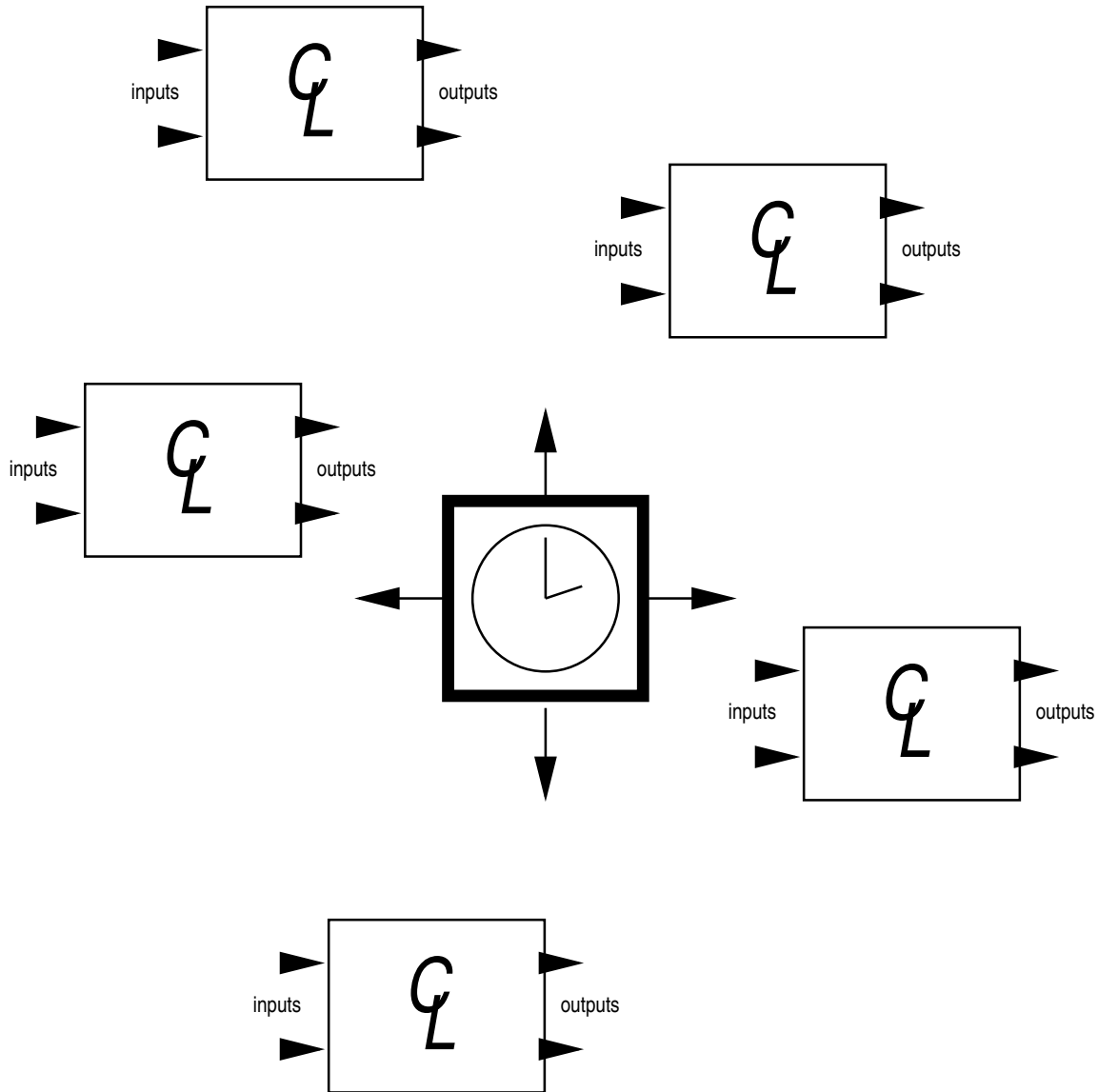
Standard method of solving the problem: Clocks.




A single central *clock* keeps time for all the function units.

Clocking discipline

A simple clocking discipline...

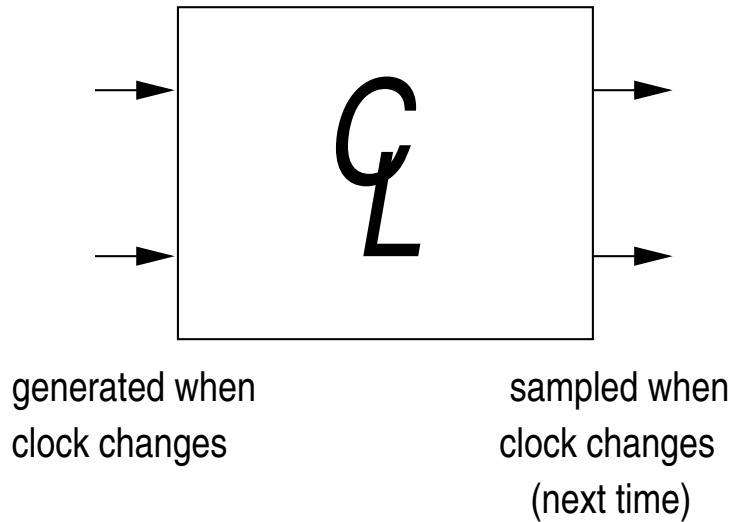

 
“Edge-triggered” clocks (used a lot in TTL circuits).



This exact approach not so good for CMOS, but it's on the right track.

A simple basic element

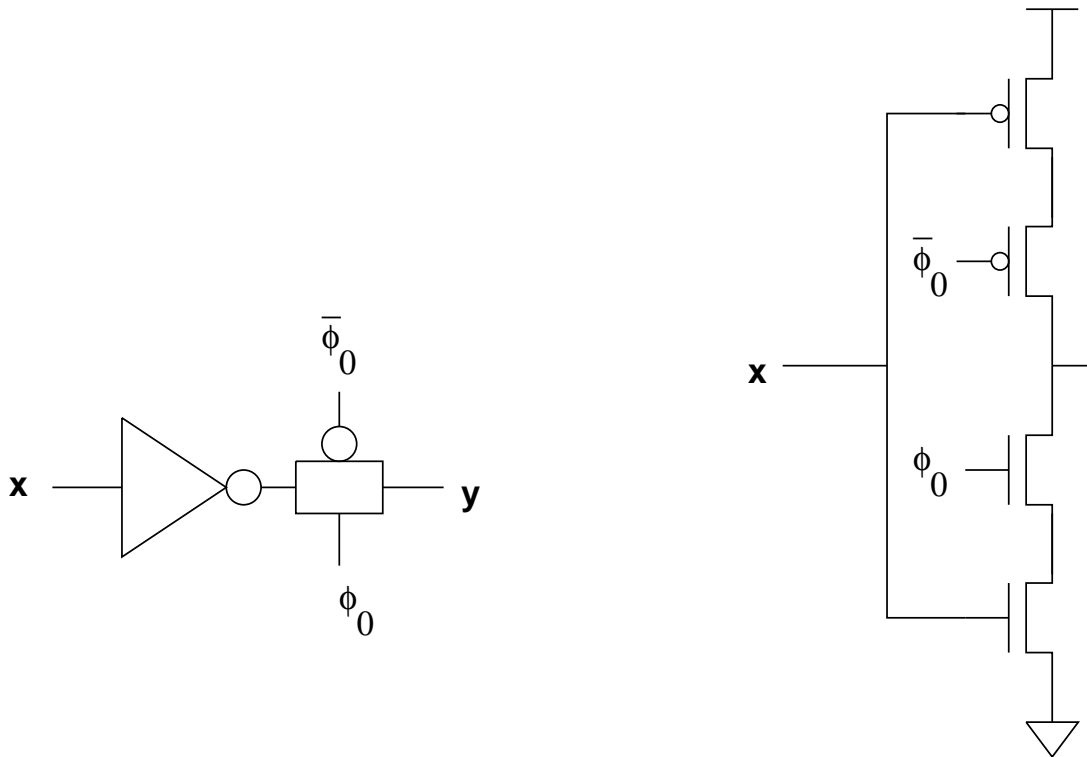To choose our clocking approach, we need to examine the basic building blocks.



This behaves like a three-state D-type latch...


In CMOS, we can do this with very few transistors. Why? (For comparison: TTL D-type flip-flop has about 20-30 transistors...)

Output might float...

When can we float?

But there are conditions...

 - Wire must be a good capacitor to ground.



- We need a gate to store charge on.
- Avoid trying to store charge on nodes with larger and leakier sources and drains...

Staticizer, also called Keeper

$$Bu \rightarrow y\uparrow$$

$$Bd \rightarrow y\downarrow$$

- “Floating”: no path to Vdd or GND when $\neg Bu \wedge \neg Bd$
- What happens to the charges on the output node when the node is floating?
- **Add another path to Vdd and GND**

$$Bu \vee Cu \rightarrow y\uparrow$$

$$Bd \vee Cd \rightarrow y\downarrow$$

- Simplest solution: $Cu = y$ and $Cd = \neg y$

$$Bu \vee \neg y_- \rightarrow y\uparrow$$

$$Bd \vee y_- \rightarrow y\downarrow$$

with $y_- = \neg y$

Standard Staticizer

- Problem: “Fight”
- Remember the requirement of non-interference between complementary PRS

$$Bu \vee \neg y_- \rightarrow y\uparrow$$

$$Bd \vee y_- \rightarrow y\downarrow$$

- Now we can have Bu and y_- or Bd and $\neg y_-$ true at the same time


Fight in Staticizer

- Suppose we want to switch y to zero
- $i1$ moves $V(y)$ towards VDD
- $i2$ moves $V(y)$ towards GND
- Strongest current wins the fight. We want $i2$ to win
- Make $i1$ very small by making pFET very resistive
- We say that the feedback inverter is “weak”

Basic clocking strategy

We design our combinational logic as in labs 1 and 2.

 - Surround it with latches to control when we give it data and when we sample its outputs.



What do we use for the clocks?


“One-phase” clock

MOSFETS are level-sensitive. . .

We don't know how to build (simple) edge-triggered CMOS circuits!

⇒ One-phase clocking scheme is BAD.

Consider simplest “CL” — a wire:

 

Think of it as an air lock.


- If we open both valves at the same time, the signal can “race through” the system—it will show up a clock cycle early at the output, sending the rest of the system into confusion.

Clocking disciplines

The one-phase clock demands a strict *clocking discipline*.

E.g.,

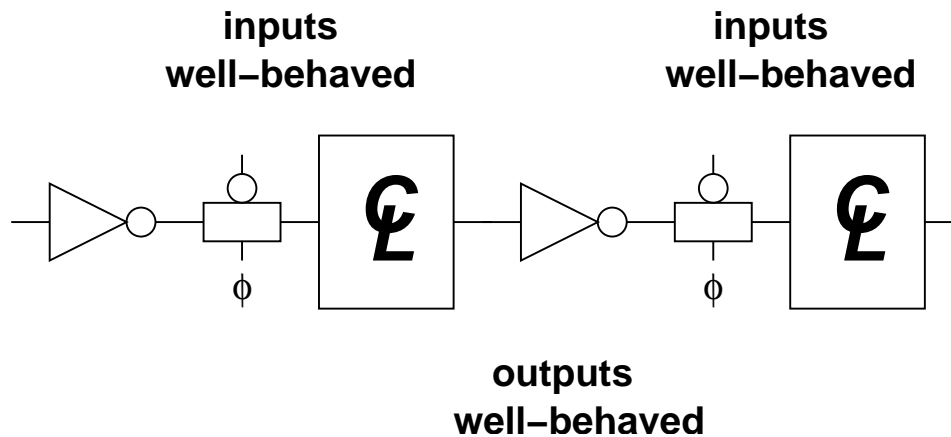- CL must hold its value constant at the old value while the clock pulse is true.
- CL must produce its new value by the time the second clock pulse comes around.




If I can guarantee this for each part of the circuit, I know it will work for the circuit as a whole!


Doesn't this seem familiar?

- “Logic levels” ?
- What do I mean by “done” anyhow?

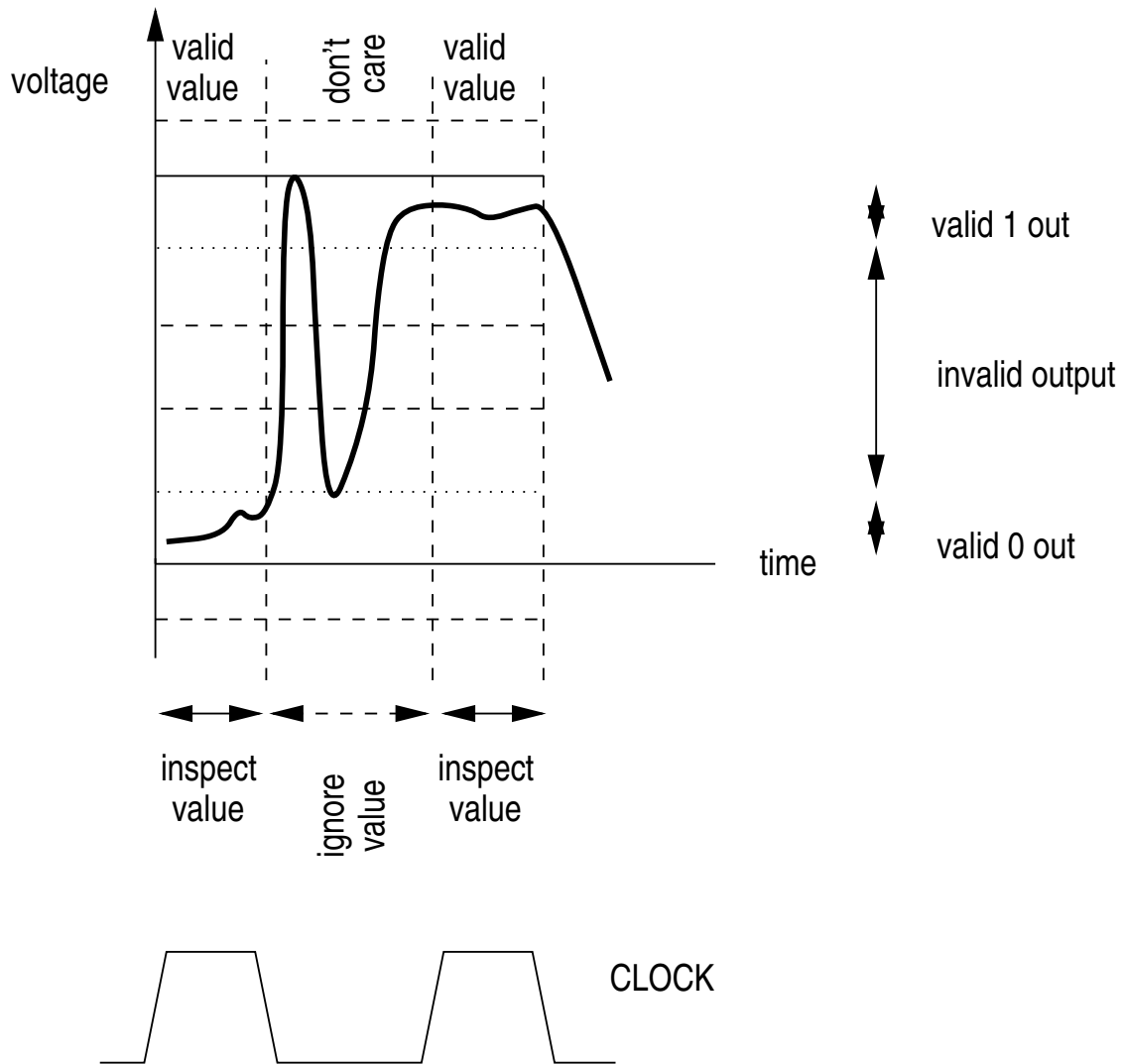Actually it's the same thing as logic levels, except in time rather than in voltage. . .



The problem—One-phase

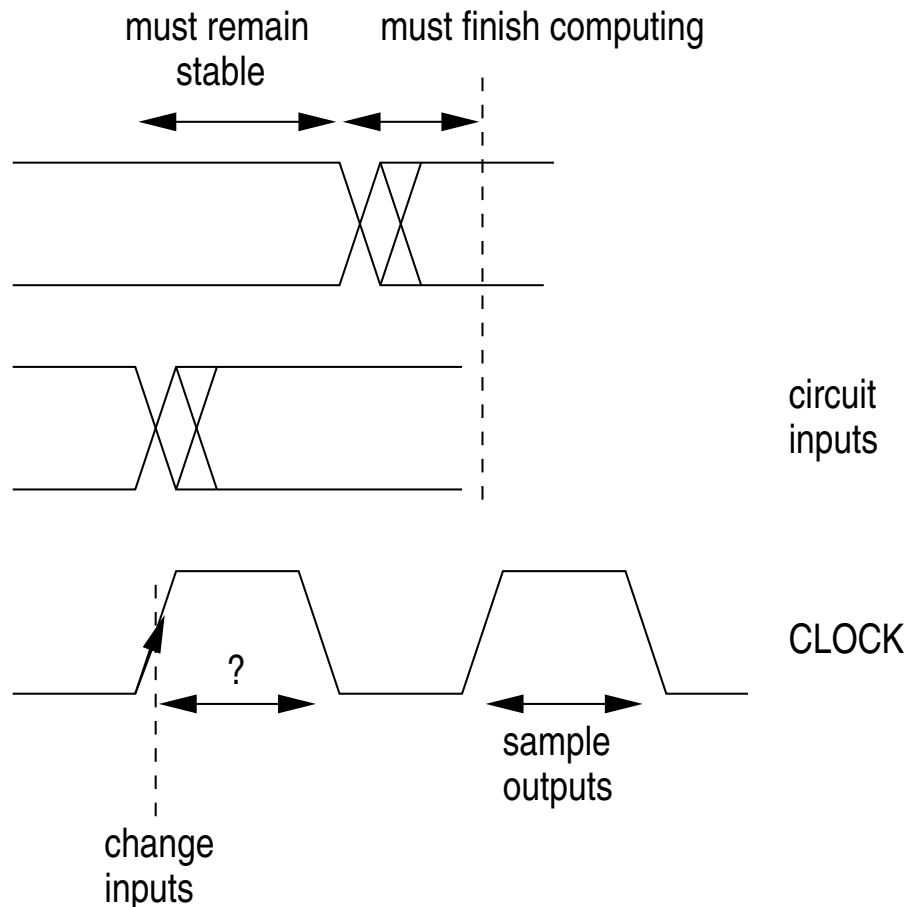

- Too slow and we won't meet constraint on the right—won't be done computing when the clock samples the output.
- Too fast and we mess up the sampling of the previous value.

Two-sided constraint! *Very* difficult to deal with.
(But fast!)

“Two-phase” (nonoverlapping) clock

What we want is a timing discipline that is easier to obey.

- Sample inputs during one clock phase ϕ_0 .
- Produce outputs during one clock phase ϕ_1 .


ϕ_0 and ϕ_1 are not to overlap—there is no race.

- If it doesn't work because our circuits are too slow, just slow down the clock.
- Very “safe” and conservative.

A picture—Nonoverlapping clock

Two nonoverlapping phases.

 - The gap between the phases takes care of clock *skew* in the system.



And when neither clock is asserted?


- State holding! (This is where the CMOS capacitors come in.)

Obvious disadvantages compared to one-phase clock:

- Potentially lower performance.
- More clock wires.

How to do it

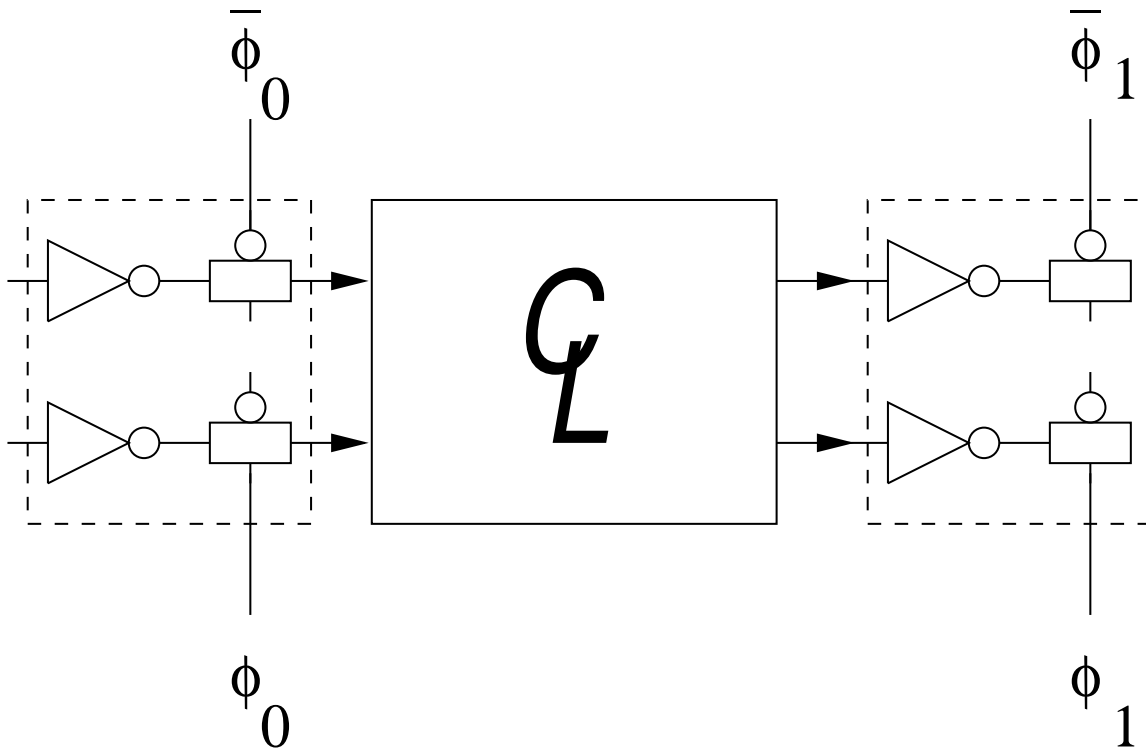
We will see this structure again and again for the rest of the term:




Of course, sometimes you may want to reverse the two.

In practice

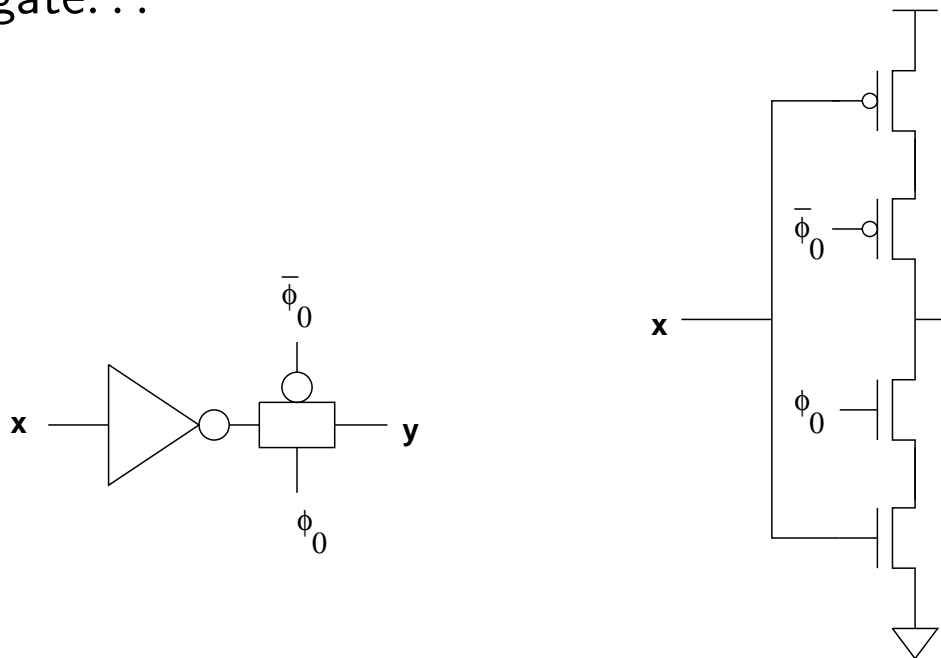We notice that we can disconnect the transistors in the pass gate. . .



 We can call this a “half latch” or “half register” —why?



This is a *shift register*.

Maintaining the timing discipline

Now that we have set up our timing discipline, we need to make sure we can maintain it.

Two potential classes of problems:

- Input changes too soon. (Back to one-phase clock.)
- Output doesn't stay put during the 00 phase.

Can either of these happen?


Unfortunately, *yes*.

Case 1. Input changes too soon—*charge sharing*.

Case 2. Output doesn't stay put—*leakage*.

Charge sharing

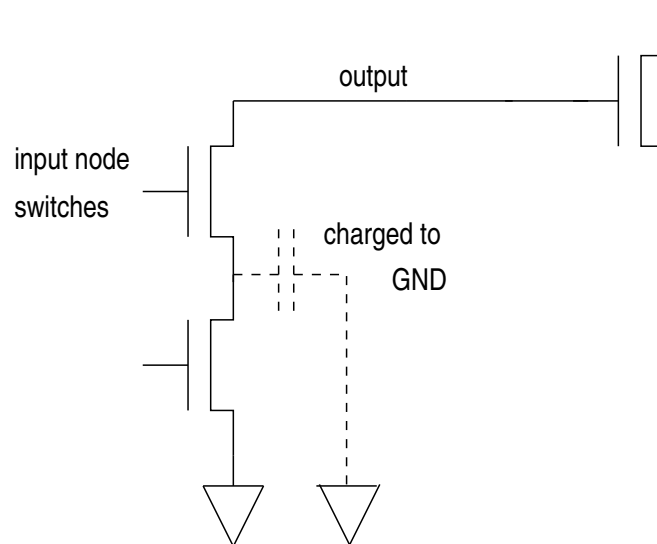When we draw the circuit diagram with the transistors looking like capacitors, it is easy to forget the p-n junction capacitance around the source and drain.




- Up to approximately $1/4$ the capacitance per unit area of gate.
- Especially bad (of course) if you use diffusion wires.
- Perimeter term—worst for small transistors.

The internal node can act like a power supply on its own if there is nothing to keep the output high! Output may switch prematurely, defeating the clocking discipline.

Staticizers

 What if the capacitor leaks? What can we do about that?




(Example weak inverter: n-transistor 3λ wide (minimum size) by at least 12 long, p-transistor 3×8 .) Use a state-holding element to hold the circuit's state. (In a sense, we are going back to the rule that the output always has to be driven.)

- Optional for nodes that are charged up on every clock cycle
- Important for easy testing.
- Essential for circuits that are not known to be charged every cycle.
- Essential for lab assignments!

Sample register designs

 
For Lab 3, you will want to know how to design registers. (Not just shift registers.)




Normally, we enforce a clocking discipline for the bus and everything connected to it. Thus, $w = (\text{write}) \wedge \phi_0$ and $r = (\text{read}) \wedge \phi_1$. (The same discipline has to be obeyed by all units connected to the bus.)

- This register isn't perfect. . .

Two that work a bit better:

 

(12T)

 

(14T)

- How do we generalize the register to have multiple inputs and/or outputs? (Not difficult.)


Register cookbook

Basic idea:

- Make sure that we drive the destination bus (won't be driven by it).
- Make sure that we are driven by source bus (won't drive it).
- Make sure all state-holding nodes are staticized.

The general idea


Imagine playing dominos:

 

Solid cells clock on ϕ_0 , dashed cells on ϕ_1 , and only neighbors communicate.

A shift register

 We can use this approach to see what we need for a shift register. . .



This is an official Lab 3 hint, but it works in general.

What happens if we do not have this alternating tiling?

Imagine the clock is *infinitely slow*—successive ϕ_0 or ϕ_1 latches are transparent at the same time!

Next Time

Next time, we will continue talking about registers and how to use them together with logic.

- What to do about charge sharing.
- More register designs.

Other tricky applications of clocks in CMOS designs. . .

- Precharge logic.
- PLAs. (Special case of precharge logic.)
- Lab 3 examples. . .